

In an a.c. circuit, the instantaneous e.m.f. and current are given by

$$e = 100 \sin 30t$$

$$i = 20 \sin \left(30t - \frac{\pi}{4} \right)$$

In one cycle of a.c., the average power consumed by the circuit and the wattless current are, respectively:

(1) 50, 10

(2) $\frac{1000}{\sqrt{2}}$, 10

(3) $\frac{50}{\sqrt{2}}$, 0

(4) 50, 0

Based on JEE Main 2018 - [123IITJEE](#)

$$P_{AV} = V_{rms} I_{rms} \cos \phi$$

$$\therefore P_{AV} = \frac{20}{\sqrt{2}} \times \frac{100}{\sqrt{2}} \cos \left(-\frac{\pi}{4} \right) = \frac{1000}{\sqrt{2}}$$

Hence, the only option possible is option (2). Further verification can be done as follows:

Let, $e = e_0 \sin(\omega t)$ and $i = i_0 \sin(\omega t + \phi)$

$$i = i_0 (\sin \omega t \cos \phi + \cos \omega t \sin \phi)$$

Or, $i = (i_0 \cos \phi) \sin \omega t + (i_0 \sin \phi) \cos \omega t$

When product of e and i is integrated over a cycle to find the average power, the $i_0 \sin \phi$ part of the current gives zero result as the integral of $\sin \omega t \cdot \cos \omega t$ over a cycle is zero. The rms current corresponding to $i_0 \sin \phi$ is the wattless current.

So, wattless current =

$$|I_{rms} \sin \phi| = \left| \frac{20}{\sqrt{2}} \sin \left(-\frac{\pi}{4} \right) \right| = 10$$

Ans: Option (2).