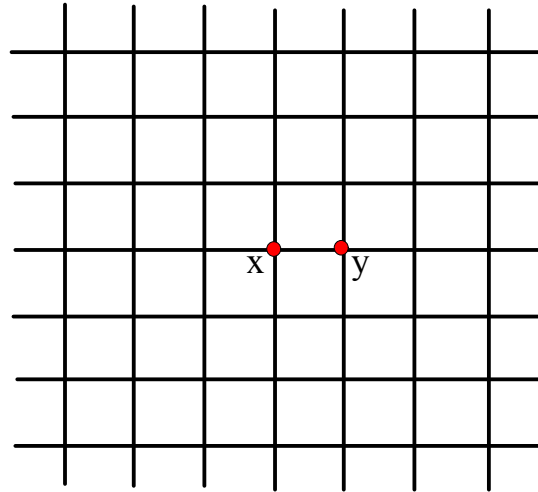


There is an infinite wire grid with square cells. The resistance of each wire between neighbouring joint connections is R . Find the equivalent resistance of the whole grid between points x and y .



Solution

Normally, resistive network problems are solved when steady-state is reached after the battery is connected. However, for this problem let us find equivalent resistance by transient-state analyses. Resistance is not affected whether it is steady-state or transient-state.

Let us place charge Δq at point x alone. This charge will get distributed equally in four directions. Charge that flows towards $y = \frac{\Delta q}{4}$.

Likewise, let us place charge $-\Delta q$ at point y alone. This charge will get distributed equally in four directions. Charge that flows towards $x = -\frac{\Delta q}{4}$ or charge that flows towards $y = +\frac{\Delta q}{4}$.

When charge Δq is placed at point x and charge $-\Delta q$ is placed at point y simultaneously, the charge that flows towards $y = \frac{\Delta q}{4} + \frac{\Delta q}{4} = \frac{\Delta q}{2}$.

$$V_x - V_y = i_{x \rightarrow y} R = \frac{\Delta q / 2}{\Delta t} R \dots (1)$$

$$\text{Also, } V_x - V_y = i_{total} R_{eq} = \frac{\Delta q}{\Delta t} R_{eq} \dots (2)$$

$$\text{From (1) \& (2), we have } R_{eq} = \frac{R}{2}.$$

Now, try to do this problem in similar manner by taking alternate route $x \rightarrow y$. You are welcome to share your solution via comment.

