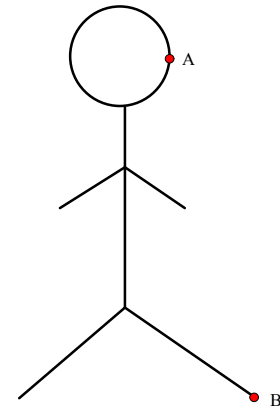



A scientist created a two-dimensional circuit made of uniform wire, which he called *manav* during his research to find the lowest resistance path in human bodies. He experimented with it by connecting it across various points across a battery. Can you help him to find the resistance between the ear* (A) of this *manav* and the toe (B)?



Take the resistance per unit length of the wire = λ ,
 Radius of head = a ,
 Length of neck = n ,
 Length of one arm = h ,
 Length of the mid-section = m ,
 Length of one leg = l .

*Assume that the length of the arc joining the ear A to the upper part of neck is $1/4^{\text{th}}$ of the circle.

Solution

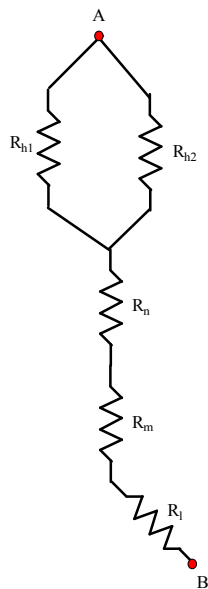

Resistances offered by both arms and one leg are not considered in the figure as they do not form part of the circuit.

$$R_{h1} = \left(\frac{3}{4} \times 2\pi a \right) \lambda = \frac{3}{2} \pi a \lambda$$

$$R_{h2} = \left(\frac{1}{4} \times 2\pi a \right) \lambda = \frac{1}{2} \pi a \lambda$$

$$R_{AB} = R_{h1} \parallel R_{h2} + R_n + R_m + R_l$$

$$\therefore R_{AB} = \frac{3}{8} \pi a \lambda + n\lambda + m\lambda + l\lambda$$

$$\Rightarrow R_{AB} = \left(\frac{3}{8} \pi a + n + m + l \right) \lambda$$