
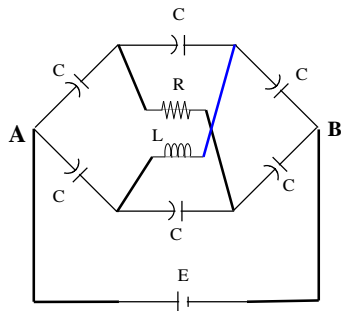


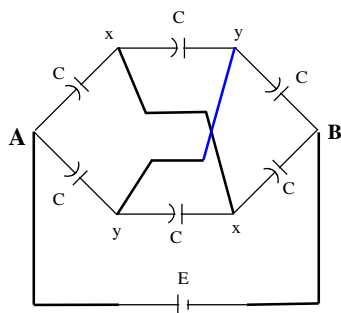What is the capacitance between points A and B under steady state? The black colour wires lie on the plane of the screen. The blue colour wire lies above the plane of the screen.




Solution

Under steady-state no current flows through both R and L and both of these will act just like wires. So, the circuit can be redrawn as,




Or,

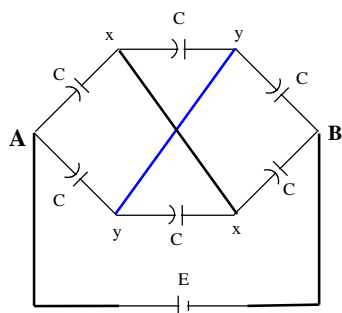


Note: Blue wire is not cutting any other wire as it is on a different plane.

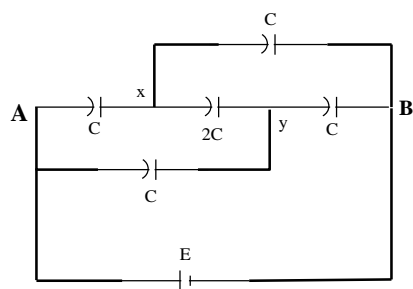
There are two capacitors across x & y whose equivalent capacitance would be $2C$.



Which across A & B is same as,

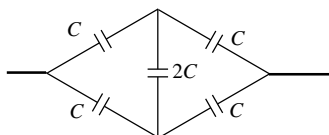

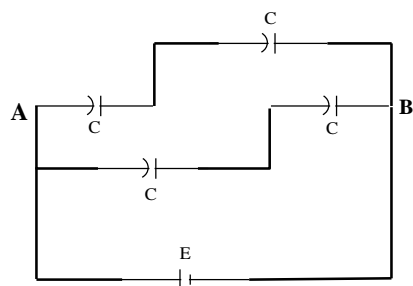Due to symmetry the capacitor $2C$ won't be charged and can be cut. The detailed proof of such situation is available in the capacitors topic in study material.



Above case is a direct application of series and parallel combination.

Answer: C